
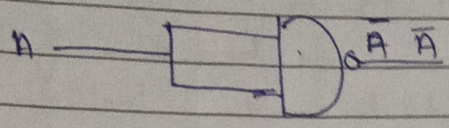


Mission 1


1) NOT

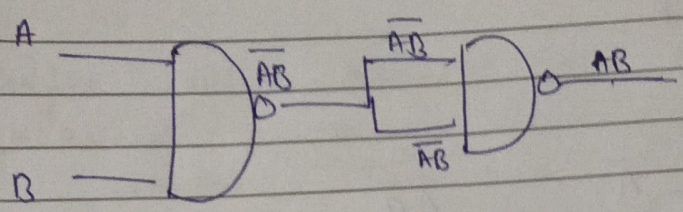

2) AND



3) OR

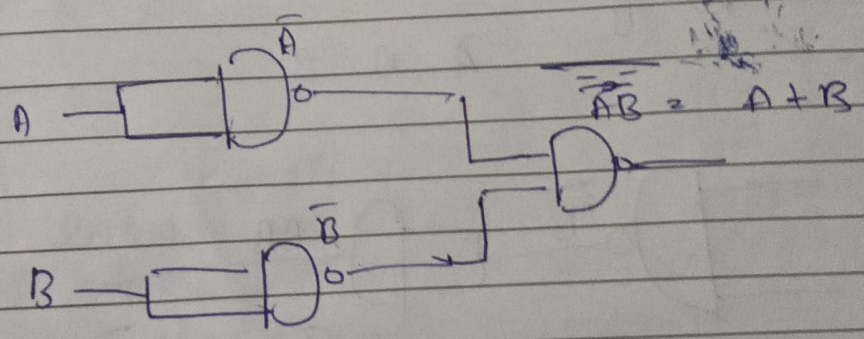


Mission - 2

truth table


q)

Input		Output	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

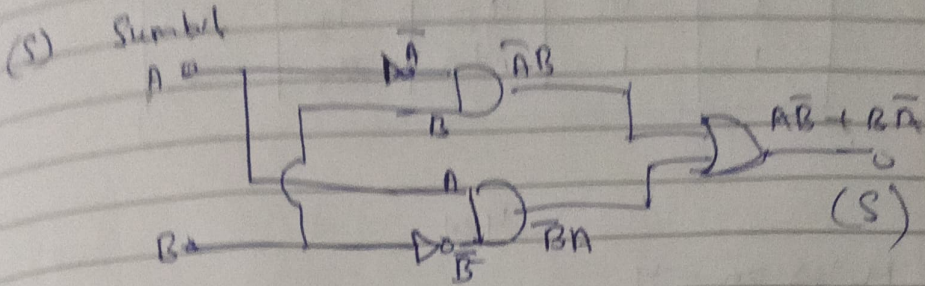
b) $S = \overline{A}B + A\overline{B}$
 $C = AB$



Carry bit

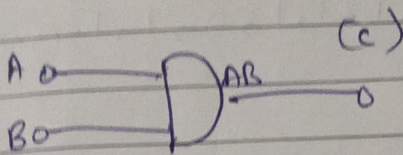

Question - 3

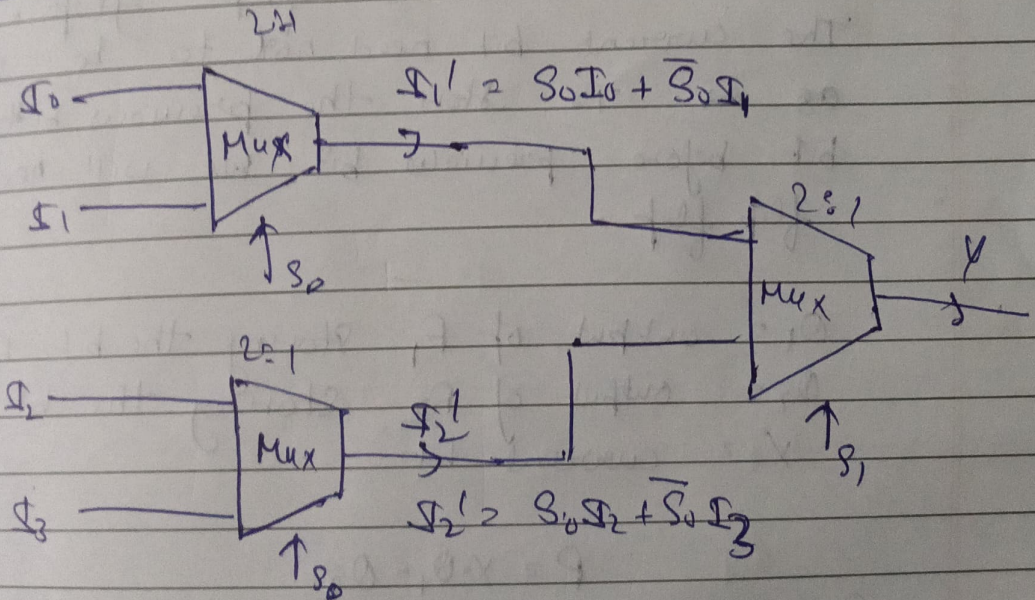

$$Y = S_1I_1' + \overline{S_1}I_2'$$

4:1 Mux truth table

S_0	S_1	I_0'	I_1'	Y (output)
0	0	I_0	I_3	I_0
0	1	I_1	I_3	I_1
1	0	I_0	I_2	I_2
1	1	I_0	I_2	I_0

4:1

Mission - 4

a) Input stream
0, 1, 1, 1, 0, 1, 1, 1, 0

output
0, 0, 0, 1, 0, 0, 0, 1, 0



We would need 2 flip flop.
The current bit need not to be stored
as ~~as~~ To store the previous bit and
bit before previous bit we will need two
flip flop.

Q_1 = output of F_1 storing the bit 1 cycle old
 Q_2 = output of F_2 storing the bit 2 cycle old
 X = current bit

$$P = X \cdot Q_1 = Q_2$$

So when when

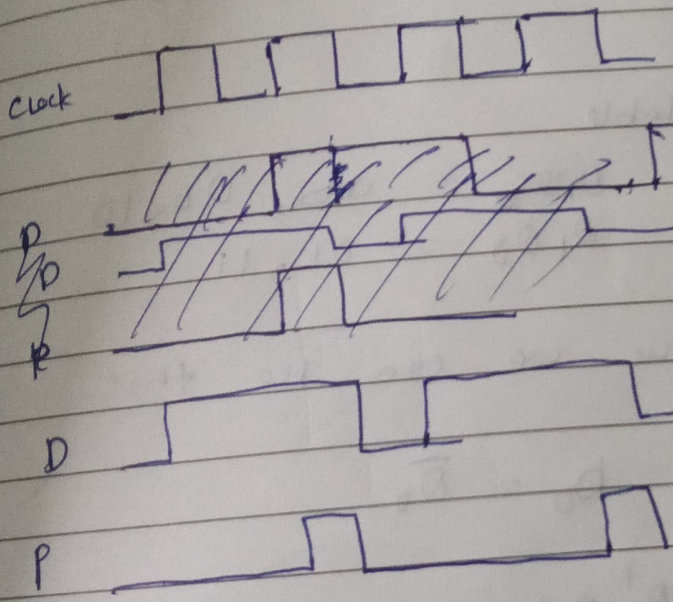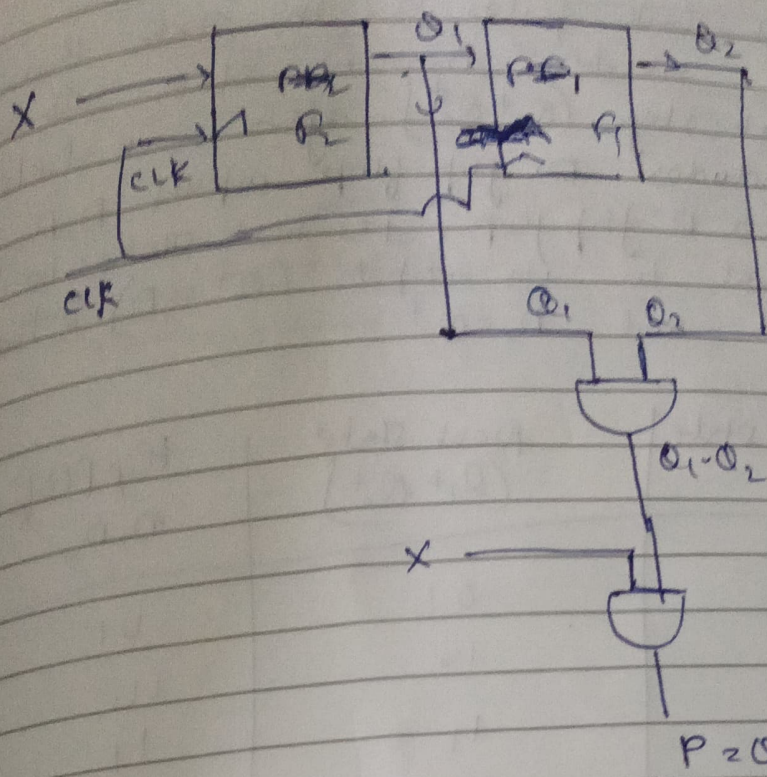$X = 1, Q_1 = 1, Q_2 = 1$
only then $P = 1$



Mission - 5

a) After 1 clock pulse, the state transition Table relates current state $(Q_1 Q_0)$ to next state $(Q_1^+ Q_0^+)$ after one clock pulse. It includes D flip-flop inputs $D_1 D_0$. Since for a D flip-flop, the next state is equal to its input ($Q^+ = D$). Therefore, $D_1 = Q_1^+$ and $D_0 = Q_0^+$.

Current state $Q_1 Q_0$	Next state $(Q_1^+ Q_0^+)$	Flip Flop $D_1 D_0$
00	01	01
01	10	10
10	11	11
11	00	00

b) from the table
 $D_0 = 1$ $Q_1 Q_0 = 00, 10$
 $D_0 = 0$ $Q_1 Q_0 = 01, 11$

from above we can see that -

$$D_0 = \bar{Q}_0$$

$$D_1 = 0 \quad Q_1^+ Q_0^+ = 00, 11$$

$$D_1 = 1 \quad Q_1^+ Q_0^+ = 01, 10$$

$$D_1 = Q_1 \bar{Q}_0 + \bar{Q}_1 Q_0$$

(XOR)

